

Workshop 01: Create a Simplified Buck Converter with Simscape Electrical

Goal

Complete and simulate an open-loop DC-DC buck converter in Simulink using Simscape Electrical. This simplified workshop follows the clip

`01_Create_Buck_Simscape_Elec_Simplify.mp4` .

Start from:

`Create_Buck_Simscape_Elec_Simplify.slx`

Finish with a model that matches:

`Create_Buck_Simscape_Elec_Simplify_finished.slx`

The starting model already contains the command, measurement, source, reference, solver, and scope blocks. In this clip, participants complete the physical buck converter power stage and verify the simulation result.

By the end of this workshop, participants should be able to:

- Identify the prepared Simulink and Simscape blocks in the starting model.
- Add the missing buck converter power-stage components.
- Connect the MOSFET, diode, inductor, capacitor, and load resistor correctly.
- Drive the MOSFET with the existing PWM physical signal.
- Measure output current and voltage using the prepared sensors and Scope.
- Run the simulation and confirm the expected buck converter output.

Prerequisites

- MATLAB with Simulink.
- Simscape.
- Simscape Electrical.
- Basic understanding of a buck converter: switch, diode, inductor, capacitor, and load.

Starting Model

Open `Create_Buck_Simscape_Elec_Simplify.slx` .

The model already includes:

Existing Block	Purpose
DC Voltage Source	Provides the input voltage
Constant	Provides the duty-cycle command
PWM	Converts duty cycle into a pulse-width-modulated signal
Simulink-PS Converter	Converts the PWM signal into a physical signal for the MOSFET gate
Current Sensor	Measures output/load current
Voltage Sensor	Measures output voltage
Two PS-Simulink Converter blocks	Convert physical sensor outputs to Simulink signals
Scope	Displays current and voltage
Electrical Reference	Provides the electrical ground/reference
Solver Configuration	Required for the Simscape physical network

The starting model is intentionally incomplete. The missing pieces are the switching device, freewheeling diode, inductor, output capacitor, and load resistor.

Reference Values

Use these values during the workshop:

Item	Value
DC input voltage	50 V
Initial duty cycle in starting model	0.8
Final duty cycle in finished model	0.5
PWM period	1e-5 s
Inductor	3e-3 H
Inductor resistance	0 Ohm
Capacitor	1e-5 F
Load resistor	1 Ohm
Diode on resistance	0.3 Ohm
Diode off conductance	1e-8 S
MOSFET off conductance	1e-6 1/Ohm
Simulation stop time	0.5 s

Expected ideal steady-state output voltage before changing duty cycle:

$$V_{out} = \text{Duty} * V_{in} = 0.8 * 50 = 40 \text{ V}$$

Expected ideal steady-state output voltage after changing duty cycle to match the finished model:

$$V_{out} = \text{Duty} * V_{in} = 0.5 * 50 = 25 \text{ V}$$

The simulated voltage may not be exactly **40 V** or **25 V** because the model includes non-ideal switching and diode parameters, but it should be close to the expected buck converter behavior.

Blocks to Add

Add these blocks to the starting model.


Block	Library Path	Main Setting
MOSFET (Ideal, Switching)	Simscape > Electrical > Semiconductors & Converters	Goff = 1e-6 1/Ohm
Diode	Simscape > Electrical > Semiconductors & Converters	Ron = 0.3 Ohm , Goff = 1e-8 S
Inductor	Simscape > Electrical > Passive	L = 3e-3 H , r = 0 Ohm
Capacitor	Simscape > Foundation Library > Electrical > Electrical Elements	C = 1e-5 F
Resistor	Simscape > Foundation Library > Electrical > Electrical Elements	R = 1 Ohm

Workshop Procedure

Follow this order in the workshop:

Review starting model -> Add switching stage -> Add diode and inductor
-> Add output filter/load -> Connect measurements -> Check infrastructure
-> Change duty cycle -> Configure and save -> Simulate and inspect

1. Open and review the starting model

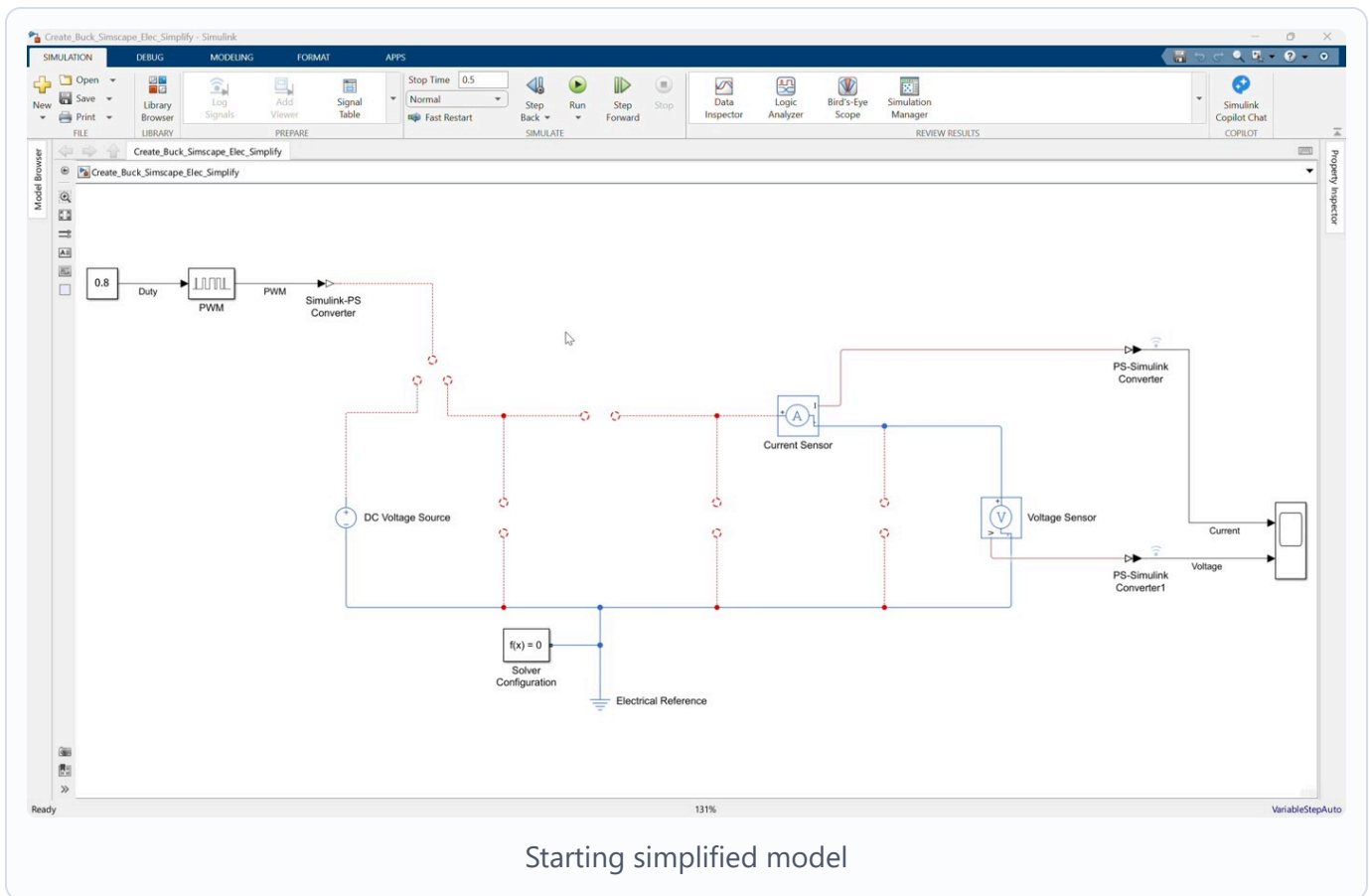

Video screenshot: the prepared starting model before completing the buck converter power stage.

1. Open `Create_Buck_Simscape_Elec_Simplify.slx`.
2. Confirm that the following prepared blocks are already present:

- DC Voltage Source
- Constant
- PWM
- Simulink-PS Converter
- Current Sensor
- Voltage Sensor
- Two PS-Simulink Converter blocks
- Scope
- Electrical Reference
- Solver Configuration

1. Observe that the source positive terminal, current sensor input, and PWM physical-signal output are not yet connected into a complete converter circuit.

2. Add the MOSFET switch

1. Add a MOSFET (Ideal, Switching) block.
2. Set or confirm the MOSFET off conductance:

$$G_{off} = 1e-6 \text{ 1/Ohm}$$

1. Connect the positive terminal of the DC Voltage Source to the MOSFET drain terminal D.
2. Connect the physical-signal output of the Simulink-PS Converter to the MOSFET gate terminal G.
3. Leave the MOSFET source terminal S available as the switching node.

3. Add the freewheeling diode

1. Add a Diode block.
2. Set the diode parameters:

$$R_{on} = 0.3 \text{ Ohm}$$

$$G_{off} = 1e-8 \text{ S}$$

1. Connect the diode negative terminal to the MOSFET source terminal S.
2. Connect the diode positive terminal to the electrical return node.

The diode provides the freewheeling path when the MOSFET is off.

4. Add the inductor

1. Add an Inductor block.
2. Set the inductor parameters:

$$L = 3e-3 \text{ H}$$

$$r = 0 \text{ Ohm}$$

1. Connect the inductor input terminal to the MOSFET source/switching node.
2. Connect the inductor output terminal to the positive side of the output current path.

In the finished model, the inductor output connects to the current sensor input and the capacitor positive terminal.

5. Add the output capacitor

1. Add a **Capacitor** block.
2. Set the capacitance:

$$C = 1e-5 \text{ F}$$

1. Connect the capacitor positive terminal to the output node after the inductor.
2. Connect the capacitor negative terminal to the electrical return node.

The capacitor smooths the switched waveform at the converter output.

6. Add the load resistor


1. Add a **Resistor** block.
2. Set the resistance:

$$R = 1 \text{ Ohm}$$

1. Connect the resistor positive terminal to the current sensor output/output voltage node.
2. Connect the resistor negative terminal to the electrical return node.

The resistor represents the load of the buck converter.

7. Complete the measurement connections

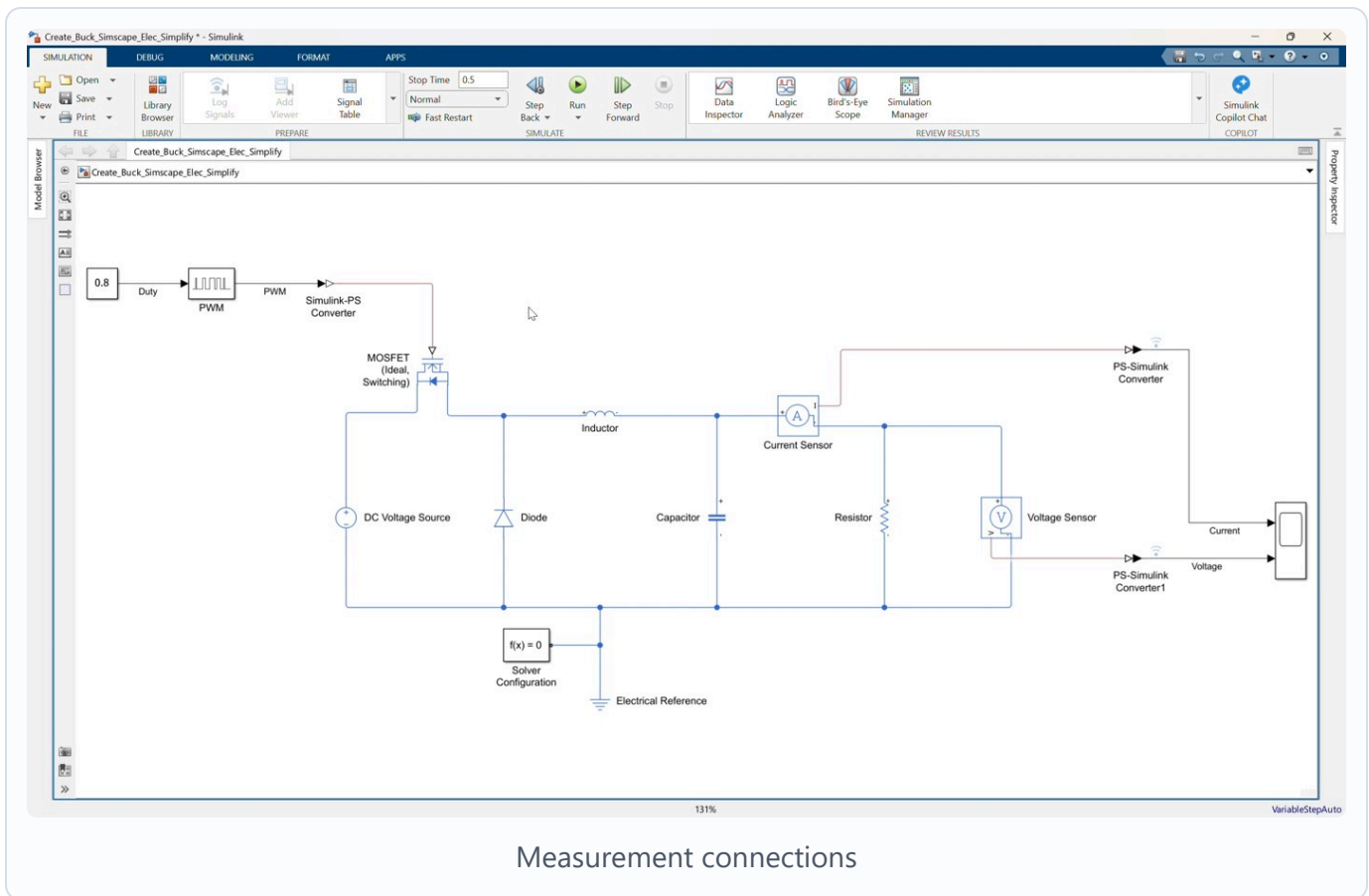


Video screenshot: current and voltage measurement paths connected to the Scope.

1. Confirm the **Current Sensor** is in series between the output capacitor side of the inductor and the load resistor.
2. Confirm the current sensor physical-signal output is connected to the first **PS-Simulink Converter**.
3. Confirm the first **PS-Simulink Converter** output is connected to Scope input 1.
4. Confirm the **Voltage Sensor** is connected across the output node and electrical return node.
5. Confirm the voltage sensor physical-signal output is connected to the second **PS-Simulink Converter**.
6. Confirm the second **PS-Simulink Converter** output is connected to Scope input 2.

Suggested Scope signal order:

Scope input 1: Output current
Scope input 2: Output voltage

8. Check the Simscape infrastructure

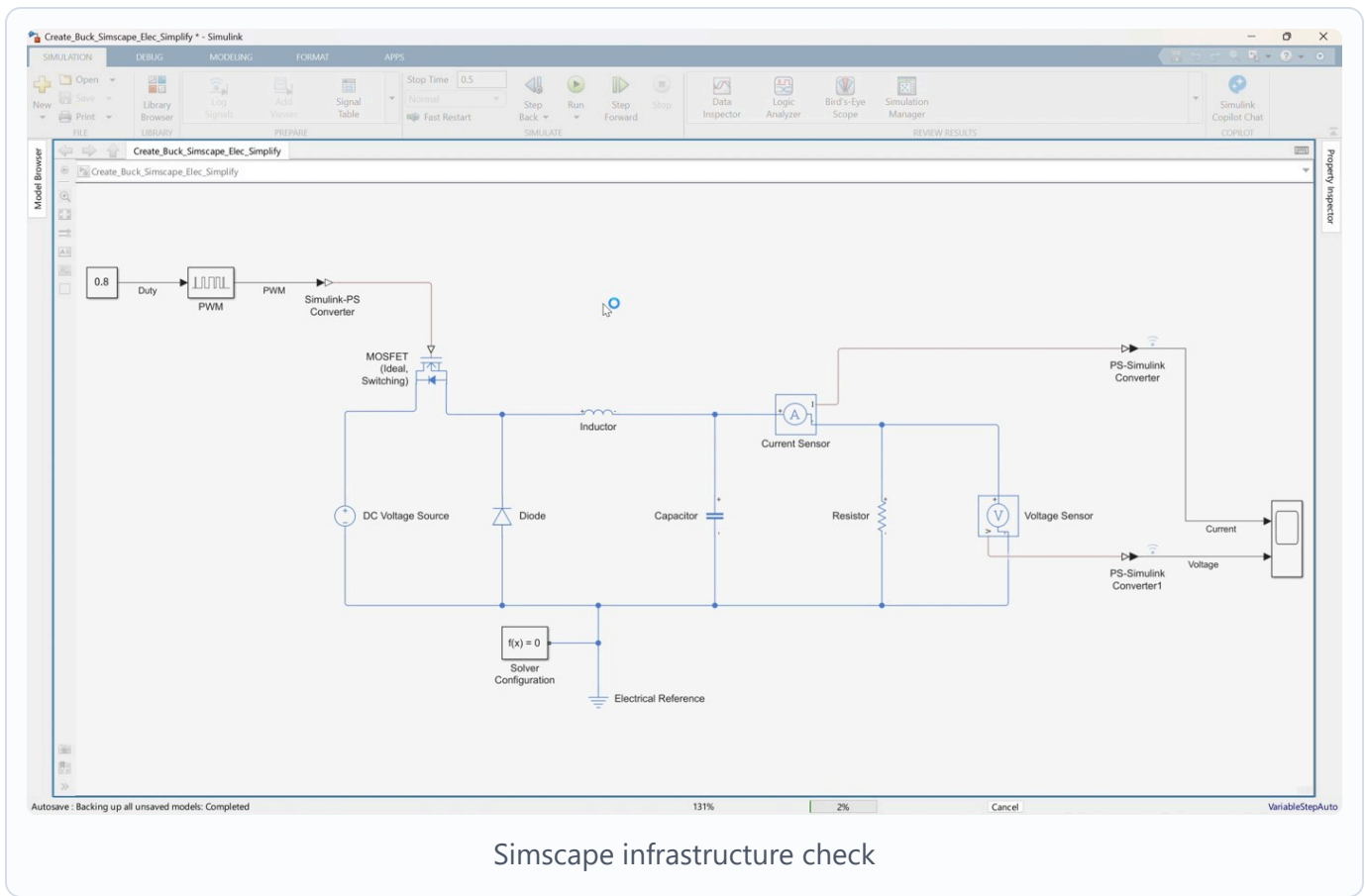


Video screenshot: completed physical network with electrical reference and solver configuration.

1. Confirm the **Electrical Reference** is connected to the converter return node.
2. Confirm the **Solver Configuration** block is connected to the same physical electrical network.
3. Confirm the negative terminal of the **DC Voltage Source**, diode return, capacitor return, resistor return, voltage sensor return, electrical reference, and solver configuration all share the same return node.

The model will not simulate correctly unless the physical network has both an electrical reference and solver configuration.

9. Set the duty-cycle command

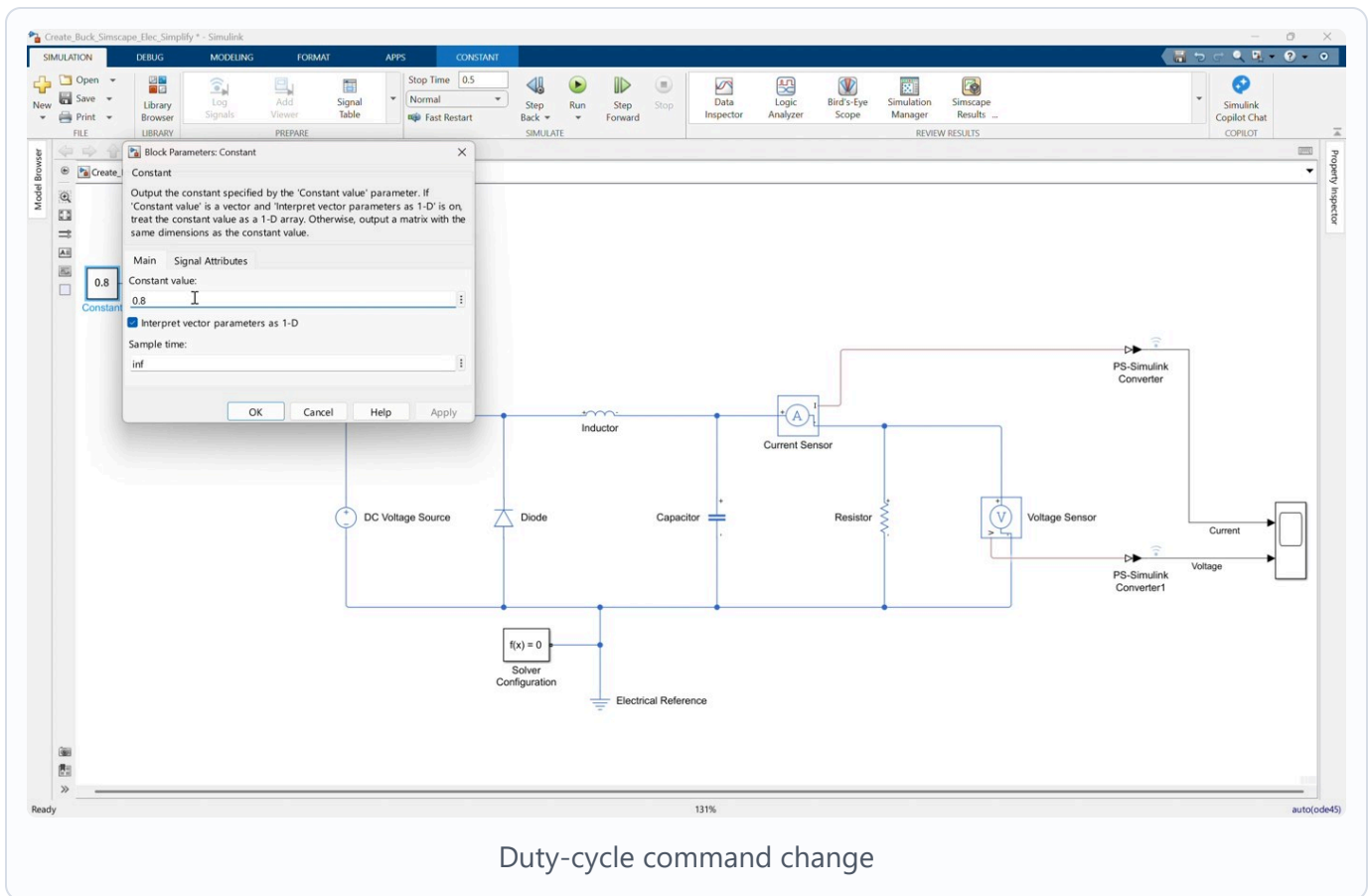

Video screenshot: changing the Constant block duty-cycle value from the initial case to the final case.


1. Open the **Constant** block.
2. Confirm the starting value is **0.8**.
3. Explain that this initial value would produce an ideal buck output of:

$$V_{out} = 0.8 * 50 = 40 \text{ V}$$

1. Change the **Constant** value to **0.5**.
2. Confirm the **Constant** output is connected to the **PWM** block.
3. Confirm the **PWM** block output is connected to the **Simulink-PS Converter**.

This final command produces a 50 percent duty-cycle PWM signal for the MOSFET and matches **Create_Buck_Simscap_Elec_Simplify_finished.slx**.

10. Configure and save the model

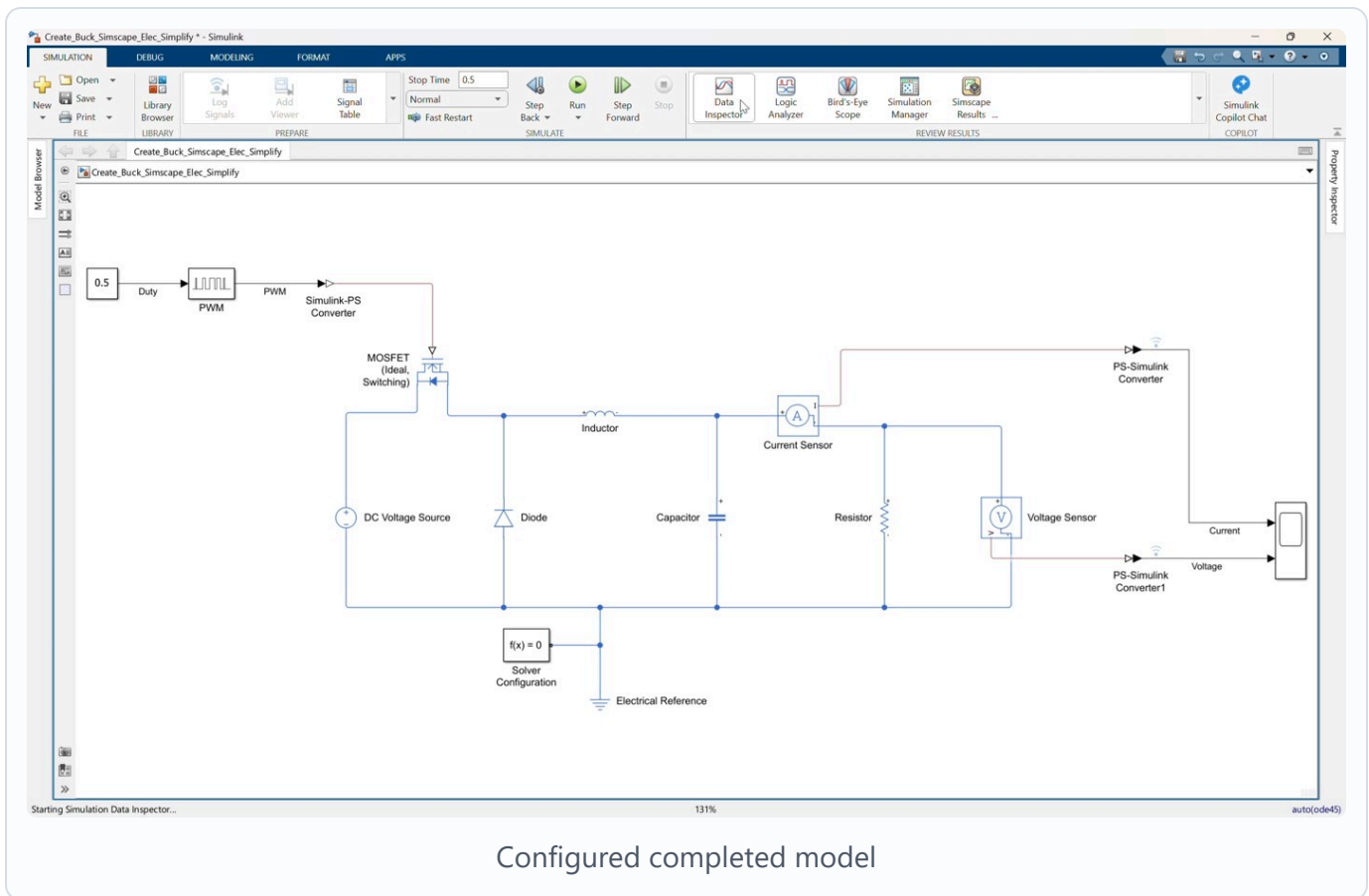

Video screenshot: completed buck converter model before the final simulation check.

1. Set the simulation stop time to:

0.5

1. Review the circuit from left to right:


DC source -> MOSFET -> Inductor -> Current Sensor -> Load

1. Save the completed model.

If you want to compare against the provided completed file, open:

Create_Buck_Simscap_Elec_Simplify_finished.slx

11. Simulate and inspect the result

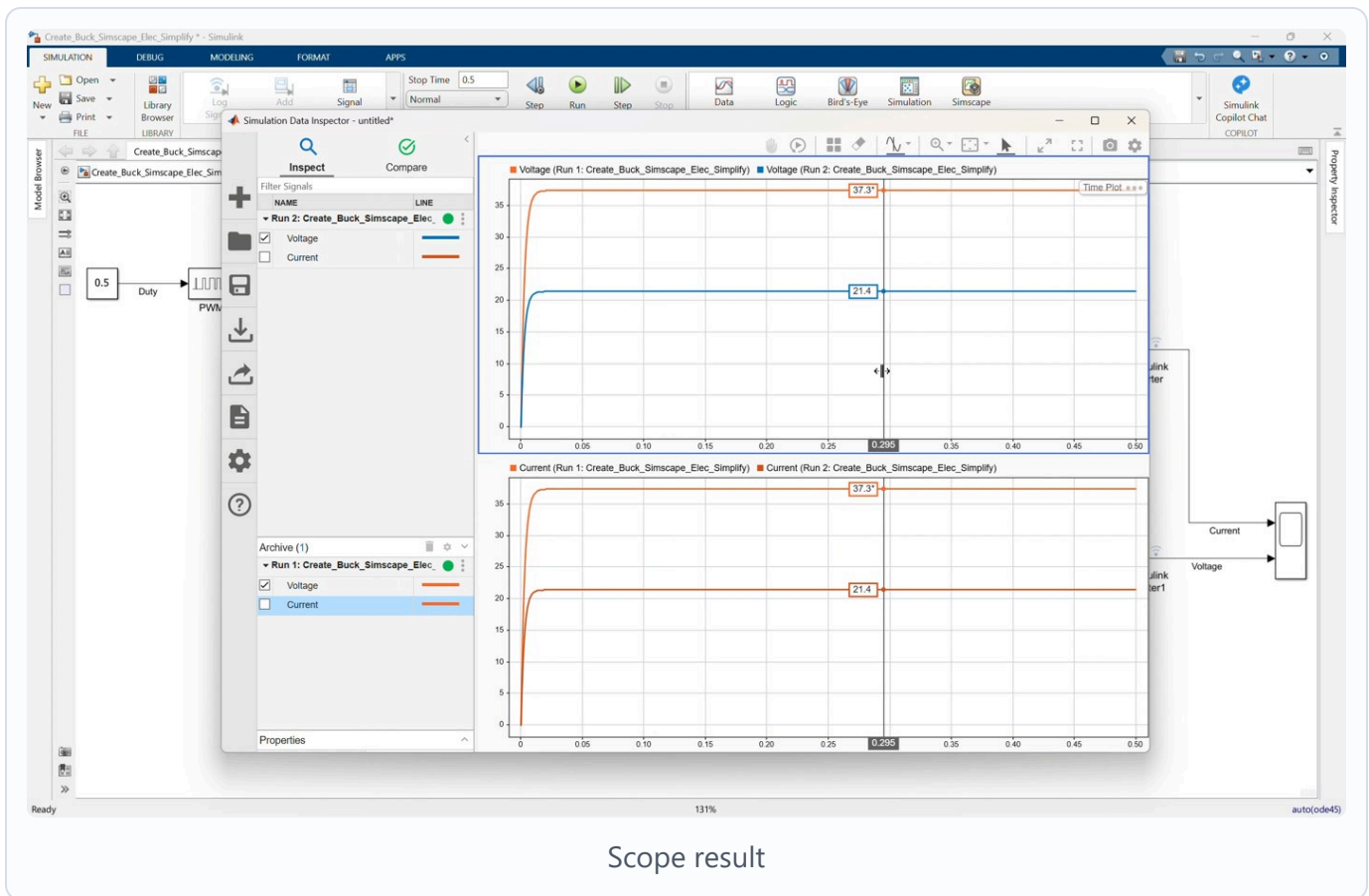

Video screenshot: Simulation Data Inspector result after running the completed model.

1. Click Run.
2. Open the **Scope**.
3. Confirm the current signal appears on Scope input 1.
4. Confirm the voltage signal appears on Scope input 2.
5. Compare the output voltage against the ideal estimate:

$$V_{out} = 0.5 * 50 = 25 \text{ V}$$

The voltage should rise toward the expected buck converter output level, with transient behavior at startup.

Suggested Instructor Flow

1. Start by explaining that the simplified model already contains the command and measurement infrastructure.

2. Ask participants to identify which blocks are already prepared and which power-stage components are missing.
 3. Leave the initial duty cycle at `0.8` while completing the circuit.
 4. Add and connect the MOSFET first so participants can identify the switching node.
 5. Add the diode and explain the freewheeling path.
 6. Add the inductor, capacitor, and resistor to complete the output stage.
 7. After the wiring check, ask participants to estimate the output for `Duty = 0.8`.
 8. Change the duty cycle to `0.5` so the model matches the finished file.
 9. Run the model and compare the Scope result with the expected `25 V`.
-

Participant Exercise

After completing the finished model, ask participants to compare the two duty-cycle cases:

1. Run the model with the final duty cycle `0.5`.
2. Confirm the expected ideal output voltage is approximately `25 V`.
3. Change the duty cycle back to `0.8`.
4. Predict the new ideal output voltage.
5. Run the simulation again.
6. Compare the Scope result with the estimate.

Expected ideal value:

$$V_{out} = 0.8 * 50 = 40 \text{ V}$$

Troubleshooting

Symptom	Likely Cause	Fix
Model does not run	Missing or disconnected Solver Configuration	Connect Solver Configuration to the physical electrical network
Electrical network error	Missing or disconnected Electrical Reference	Connect Electrical Reference to the return node
MOSFET does not switch	PWM physical signal is not connected to MOSFET gate	Connect Simulink-PS Converter output to MOSFET G
Source positive terminal is still open	MOSFET drain is not connected	Connect DC Voltage Source positive terminal to MOSFET D
No output voltage	Inductor, resistor, or capacitor output node is incomplete	Check the output node and return-node wiring
Scope has no current or voltage signal	Sensor physical outputs are not connected to converters	Check both PS-Simulink Converter connections
Output voltage is unexpected	Duty cycle, source voltage, diode orientation, or MOSFET orientation is incorrect	Check Duty = 0.5 for the finished model, Vin = 50 V, and the switching-node connections

Reference Model Check

The completed model should follow this connection structure:

Constant -> PWM -> Simulink-PS Converter -> MOSFET gate
DC Voltage Source positive -> MOSFET drain
MOSFET source -> switching node
Diode from return node to switching node
Switching node -> Inductor -> Current Sensor -> output/load node
Output/load node -> Resistor -> return node
Inductor output side -> Capacitor -> return node
Output/load node -> Voltage Sensor positive
Voltage Sensor negative -> return node
Current Sensor signal -> PS-Simulink Converter -> Scope input 1
Voltage Sensor signal -> PS-Simulink Converter -> Scope input 2
Electrical Reference and Solver Configuration connected to the return node